



Circuits

Part 5



Defining Boolean Logic

"Want to define it?"
"True."

Defining Boolean Logic

- Let's look at what exactly Boolean logic is in context of data types and functions
- Once we define the Boolean Data type, we can apply it to other systems



4/18/2017

Sacramento State - Cook - CSc 28 - Spring 2017

3

Boolean Logic and Sets

- Boolean values only have two possible values: **True** and **False**
- So, the set of values can be specified as **{True, False}** or, alternatively, as **{1, 0}**


4/18/2017

Sacramento State - Cook - CSc 28 - Spring 2017

4

Functions

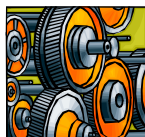- Also recall functions from earlier
- An *abstract data type* is a set of values and functions on those values
- So, we can define the data type for Boolean values



4/18/2017

Sacramento State - Cook - CSc 28 - Spring 2017

5

Defining Boolean Algebra

$S = \{0, 1\}$

$*$: $S, S \rightarrow S$ "And"
 $+$: $S, S \rightarrow S$ "Or"
' : $S, S \rightarrow S$ "Negation"

For all $x, y, z \in S$ the following is true...

4/18/2017

Sacramento State - Cook - CSc 28 - Spring 2017

6

1. Associative

$$(x + y) + z = x + (y + z)$$

$$(x * y) * z = x * (y * z)$$

4/18/2017

Sacramento State - Cook - CSc 28 - Spring 2017

7

2. Commutative

$$x + y = y + x$$

$$x * y = y * x$$

4/18/2017

Sacramento State - Cook - CSc 28 - Spring 2017

8

3. Distributive

$$x * (y + z) = (x * y) + (x * z)$$

$$x + (y * z) = (x + y) * (x + z)$$

4/18/2017

Sacramento State - Cook - CSc 28 - Spring 2017

9

4. Identity

$$x * 1 = x$$

$$x + 0 = x$$

4/18/2017

Sacramento State - Cook - CSc 28 - Spring 2017

10

5. Complement

$$x * x' = 0$$

$$x + x' = 1$$

4/18/2017

Sacramento State - Cook - CSc 28 - Spring 2017

11

Extending Boolean to Other Types

- The Boolean Data Type can be written with these 5 properties: $B = \{s, +, *, ', 0, 1\}$
- If we can show that some other type is a "Boolean algebra" if these five properties hold for all elements in S.

4/18/2017

Sacramento State - Cook - CSc 28 - Spring 2017

12

Example

Given a set U :

$S = P(U)$
 $0 = \{ \}$
 $1 = U$
 $+ = \text{set union}$
 $* = \text{set intersection}$
 $' = \text{set negation}$

4/18/2017

Sacramento State - Cook - CSc 28 - Spring 2017

13

Example

All we need to show is that:

$$(X \cup Y) \cup Z = X \cup (Y \cup Z)$$

...etc

which is what we observed with sets.

4/18/2017

Sacramento State - Cook - CSc 28 - Spring 2017

14



Boolean Algebra & Logic

From many, one

Boolean Algebra & Logic

- Boolean Algebra can be extended to other areas
- A subset of propositional logic can be put into the form of Boolean algebra



4/18/2017

Sacramento State - Cook - CSc 28 - Spring 2017

15

Propositional Logic in Boolean

$S = \{T, F\}$
 $1 = T$
 $0 = F$
 $* = \wedge$
 $+ = \vee$
 $' = \neg$

4/18/2017

Sacramento State - Cook - CSc 28 - Spring 2017

17

Applying the Five Laws

- The five laws, stated before, can be applied to propositional logic
- So, at a stroke, this gives us a very rich environment in which we can manipulate logic propositions
- So, we can treat logic as algebra

4/18/2017

Sacramento State - Cook - CSc 28 - Spring 2017

18

And, Or, Not


- All we need is: And, Or, and Not
- This is because, implications and equivalences can be expressed with them.

$$\begin{aligned}a \rightarrow b &= \neg a \vee b \\ a \leftrightarrow b &= (a \rightarrow b) \wedge (b \rightarrow a)\end{aligned}$$

4/18/2017

Sacramento State - Cook - CSc 28 - Spring 2017

19

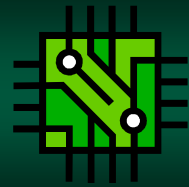


Circuits

Boolean Hardware

Circuits

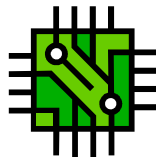- We use Boolean algebra because it can represent logical functions
- Electronic devices use logic to do their computation




4/18/2017

Sacramento State - Cook - CSc 28 - Spring 2017

21

Circuits

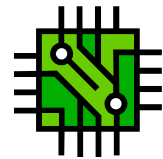- Boolean algebra gives designers tools to design & analyze solutions
- We can now look at designing electronic circuits to make simple computations



4/18/2017

Sacramento State - Cook - CSc 28 - Spring 2017

22

Two Bit Multiplier? Can we make it?



4/18/2017

Sacramento State - Cook - CSc 28 - Spring 2017

23

Designing It

- To design a circuit that multiplies two 2-bit numbers, we can use *Boolean algebra*
- We need to figure the logic – given that bits of 1 and 0 will map directly to truth values
- The result of the algebra will be the desired output

4/18/2017

Sacramento State - Cook - CSc 28 - Spring 2017

24


It Takes the Following Skills

1. Design a truth-table to represent the different inputs and the desired output
2. Convert the truth-table into a Boolean function
3. Simplify the Boolean function
4. Finally, convert it into a circuit

4/18/2017

Sacramento State - Cook - CSc 28 - Spring 2017

25

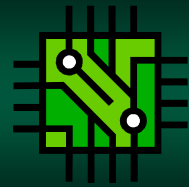


Gates

Boolean Hardware

Gates

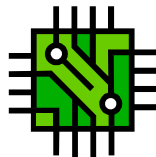- Electronic devices are made up of *gates*
- Gates take in two inputs and produce a single output
- This is how hardware is used to implement Boolean logic (or any logic)




4/18/2017

Sacramento State - Cook - CSc 28 - Spring 2017

27

Gates

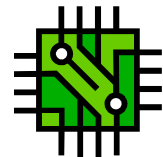- Gates can be combined into circuits with *any number of input wires* and a single output wire



4/18/2017

Sacramento State - Cook - CSc 28 - Spring 2017

28

Graphical Representation

- Gates are typically represented using graphical shapes – much like flowcharts
- There are two different competing symbol standards
- We will use the standard, distinct, symbols rather than the IEC (European) ones

4/18/2017

Sacramento State - Cook - CSc 28 - Spring 2017

29

And Gate




4/18/2017

Sacramento State - Cook - CSc 28 - Spring 2017

30

Or Gate

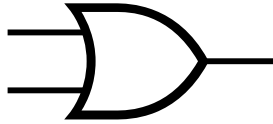


4/18/2017

Sacramento State - Cook - CSc 28 - Spring 2017

31

Not Gate

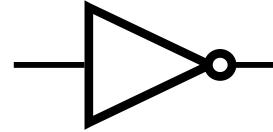


4/18/2017

Sacramento State - Cook - CSc 28 - Spring 2017

32

Exclusive Or Gate (aka XOR)

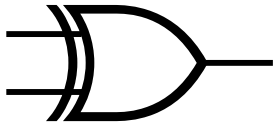

4/18/2017

Sacramento State - Cook - CSc 28 - Spring 2017

33

Some Other Gate Symbols

- There are also gate symbols for negated operators
- I won't use these much in class, but it's good to be aware of them (since they are quite common in computer engineering)
- For each, note the circle on the output line – it means "not"

4/18/2017

Sacramento State - Cook - CSc 28 - Spring 2017

34

Not And Gate (aka NAND)




4/18/2017

Sacramento State - Cook - CSc 28 - Spring 2017

35

Not Or Gate (aka NOR)

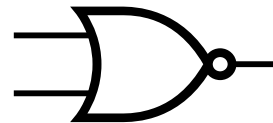


4/18/2017

Sacramento State - Cook - CSc 28 - Spring 2017

36


Not Exclusive Or Gate (aka XNOR)

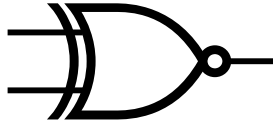

4/18/2017

Sacramento State - Cook - CSc 28 - Spring 2017

37

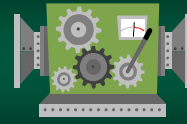


Converting Boolean to Circuits

From Logic to Wires

Converting Boolean to Circuits

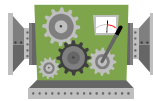- Converting from Boolean to circuits maintains a one-to-one correspondence between gates in the circuit and operators in the equation
- But, given an *arbitrary* logic table, how do we realize a circuit for it?




4/18/2017

Sacramento State - Cook - CSc 28 - Spring 2017

39

Steps

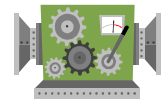1. Choose the last operation evaluated
2. Draw a gate and hook up its output
3. Goto 1 until all operations have associated gates
4. Attach the expression inputs



4/18/2017

Sacramento State - Cook - CSc 28 - Spring 2017

40

Let's Try One...



- Let's draw a gate representation for the Boolean expression below
- It is actually kinda fun!

$(a \text{ and } b) \text{ or } ((a \text{ or } b) \text{ and } c)$

4/18/2017

Sacramento State - Cook - CSc 28 - Spring 2017

41

Let's Try This...

$a \text{ xor } b = (a \text{ and } b') \text{ or } (a' \text{ and } b)$

4/18/2017

Sacramento State - Cook - CSc 28 - Spring 2017

42

Let's Try This...


Bidirectional circuit:

$$(a' + b) * (a + b')$$

4/18/2017

Sacramento State - Cook - CSc 28 - Spring 2017

43

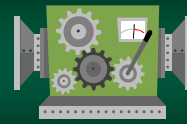


Converting Circuits to Boolean

From Logic to Wires

Converting Circuits to Boolean

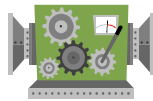- The other direction is easy too
- Any circuit can be realized as a Boolean expression using the same basic algorithm



4/18/2017

Sacramento State - Cook - CSc 28 - Spring 2017

45

Converting Circuits to Boolean


1. Pick a wire that has a known Boolean value
2. Write *on the wire* a Boolean expression for its value
3. Goto 1 until all wires are complete
4. Circuit's expression written on the circuit's output wire

4/18/2017

Sacramento State - Cook - CSc 28 - Spring 2017

46

Example Circuit

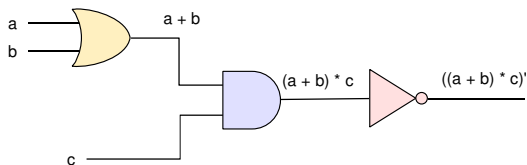

4/18/2017

Sacramento State - Cook - CSc 28 - Spring 2017

47




Creating an Arbitrary Circuit

From Truth Table to Wires

Creating an Arbitrary Circuit

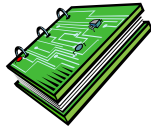- We converted between Boolean expressions and circuits
- It maintained a one-to-one correspondence between gates in the circuit and operators in the equation




4/18/2017

Sacramento State - Cook - CSc 28 - Spring 2017

49

Creating an Arbitrary Circuit

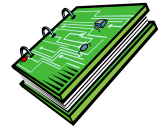- Given an arbitrary logic table, how do we realize a circuit for it?
- Simple, we look at the inputs that make it true, and write them out in an expression using or's.



4/18/2017

Sacramento State - Cook - CSc 28 - Spring 2017

50

Example: 1 Bit Add Mod 2



4/18/2017

Sacramento State - Cook - CSc 28 - Spring 2017

51

Example: 1 Bit Add Mod 2

a	b	out
0	0	0
0	1	1
1	0	1
1	1	0

4/18/2017

Sacramento State - Cook - CSc 28 - Spring 2017

52

Example: 1 Bit Add Mod 2

We want a circuit that is true when:

(a = F and b = T) or
(a = T and b = F)

out = a' * b + a * b'

4/18/2017

Sacramento State - Cook - CSc 28 - Spring 2017

53

Example 2: One Bit Adder



4/18/2017

Sacramento State - Cook - CSc 28 - Spring 2017

54

Example 2: One Bit Adder

a	b	Out ₁	Out ₀
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

4/18/2017

Sacramento State - Cook - CSc 28 - Spring 2017

55

Example: One Bit Adder (Logic)

```

out1 = (a = T and b = T)
out0 = (a = F and b = T) or
       (a = T and b = F)
    
```

4/18/2017

Sacramento State - Cook - CSc 28 - Spring 2017

56

Example: One Bit Adder (algebra)

```

out1 = a * b
out0 = a' * b + a * b'
    
```

4/18/2017

Sacramento State - Cook - CSc 28 - Spring 2017

57

Let's Draw the Circuit

- So, we convert the logic of a one-bit adder to logic
- And then to Boolean algebra
- Let's draw how it would be wired on a computer...



4/18/2017

Sacramento State - Cook - CSc 28 - Spring 2017

58



Disjunctive Normal Form

Express Logic With Ease

Disjunctive Normal Form

- Best approach to converting tables into circuits is use *Disjunctive Normal Form*
- In this form, the expressions consists of OR's (disjuncts) connecting AND sub-expressions



4/18/2017

Sacramento State - Cook - CSc 28 - Spring 2017

60

Definitions

- A *literal* is a Boolean variable v or its complement (e.g. v or v')
- A *minterm* of Boolean product $v_1 * v_2 * \dots * v_n$



4/18/2017

Sacramento State - Cook - CSc 28 - Spring 2017

61

Definitions

- Hence, a minterm is a "product" of n literals, with one literal for each variable
- An equation written only as the "OR" of minterms is in *disjunctive normal form* (also called *sum-of-products* form)

4/18/2017

Sacramento State - Cook - CSc 28 - Spring 2017

62

Algorithm

- Find the rows that indicates a 1 for output (Ignore the ones with 0 as output)
- Write a minterm for each of them
- "OR" all the minterms

4/18/2017

Sacramento State - Cook - CSc 28 - Spring 2017

63

Example

a	b	y (out)
0	0	1
0	1	1
1	0	0
1	1	0

4/18/2017

Sacramento State - Cook - CSc 28 - Spring 2017

64

Example

DNF of the table is:

$$y = (a' * b') + (a' * b)$$

For brevity, for this point on, let's write as:

$$y = a' b' + a' b$$

4/18/2017

Sacramento State - Cook - CSc 28 - Spring 2017

65

Example

We can simply using Boolean algebra:

$$\begin{aligned}
 y &= a' b' + a' b \\
 &= a' (b' + b) && \text{Distributive} \\
 &= a' (1) && \text{Complement} \\
 &= a' && \text{Identity}
 \end{aligned}$$

4/18/2017

Sacramento State - Cook - CSc 28 - Spring 2017

66

Let's Make a 2-Bit Adder


- Let's create the circuit logic for a 2-bit adder
- It will produce a 4-bit result



4/18/2017

Sacramento State - Cook - CSIS 28 - Spring 2017

67

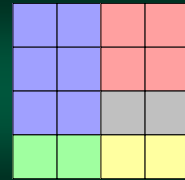


Karnaugh Maps

The Right-Brain Gets to Help

Karnaugh Maps

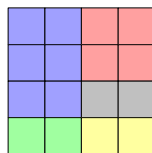- A *Karnaugh Map* (pronounced "car-no") is a visual tool to help see relations between minterms.
- A K-Map for n variables is a grid of 2^n squares




4/18/2017

Sacramento State - Cook - CSIS 28 - Fall 2016

69

Karnaugh Maps

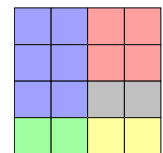- Every possible minterm of n variables is represented
- It is arranged so that every adjacent pair of squares represent two minterms



4/18/2017

Sacramento State - Cook - CSIS 28 - Fall 2016

70

Gray Code


- Each square differs in exactly one literal
- This is called *gray code*
 - the values in the table are not ordered in normal ascending order
 - makes it easy to different logical relations
- Important:** squares wrap-around to the top and sides

4/18/2017

Sacramento State - Cook - CSIS 28 - Fall 2016

71

Two-Value K-Map

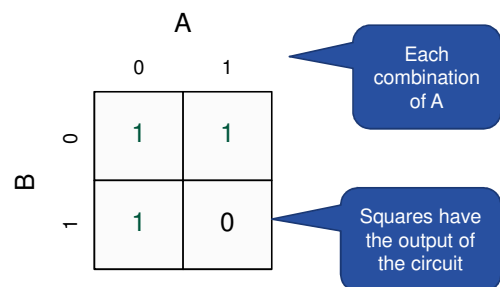

4/18/2017

Sacramento State - Cook - CSIS 28 - Fall 2016

72

Three-Variable K-Map

		AB			
		00	01	11	10
C	0	1	0	1	1
	1	0	0	1	1

4/18/2017

Sacramento State - Cook - CS&E 28 - Fall 2016

73

Four-Variable K-Map

		AB			
		00	01	11	10
CD	00	0	0	1	1
	01	1	1	0	0
	11	1	1	1	0
	10	0	1	1	0

4/18/2017

Sacramento State - Cook - CS&E 28 - Fall 2016

74

How to Use a K-Map

1. Mark the squares of a K-map corresponding to the function
2. Select a minimal set of rectangles where
 - each rectangle has a power-of-two area and is as large as possible
 - cover every marked square
3. Translate each rectangle into a single midterm and sum all these

4/18/2017

Sacramento State - Cook - CS&E 28 - Fall 2016

75

How it Works...

- The order of gray code, and the 2^n squares allow us to factor out terminals
- In a rectangle....
 - notice if a terminal changes
 - if so, it factors out to $(v + v')$ which is always true and is meaningless

4/18/2017

Sacramento State - Cook - CS&E 28 - Fall 2016

76

Example Square: 1x1

		AB			
		00	01	11	10
CD	00	1	0	0	1
	01	1	1	1	1
	11	1	1	1	1
	10	1	0	0	1

A' B' C' D

4/18/2017

Sacramento State - Cook - CS&E 28 - Fall 2016

77

Example Square: 2x1

		AB			
		00	01	11	10
CD	00	1	0	0	1
	01	1	1	1	1
	11	1	1	1	1
	10	1	0	0	1

B' C' D

4/18/2017

Sacramento State - Cook - CS&E 28 - Fall 2016

78

Example Square: 1×4

		AB				
		00	01	11	10	
CD	00	1	0	0	1	C' D
	01	1	1	1	1	
	11	1	1	1	1	
	10	1	0	0	1	

4/18/2017

Sacramento State - Cook - CS&E 28 - Fall 2016

79

Example Square: 2×2

		AB				
		00	01	11	10	
CD	00	1	0	0	1	A' D
	01	1	1	1	1	
	11	1	1	1	1	
	10	1	0	0	1	

4/18/2017

Sacramento State - Cook - CS&E 28 - Fall 2016

80

Example Square: 2×2: Wrapped

		AB				
		00	01	11	10	
CD	00	1	0	0	1	B' D
	01	1	1	1	1	
	11	1	1	1	1	
	10	1	0	0	1	

4/18/2017

Sacramento State - Cook - CS&E 28 - Fall 2016

81

Example Square: 2×2: Wrapped

		AB				
		00	01	11	10	
CD	00	1	0	0	1	B' D'
	01	1	1	1	1	
	11	1	1	0	1	
	10	1	0	0	1	

4/18/2017

Sacramento State - Cook - CS&E 28 - Fall 2016

82

Example Square: 4×2

		AB				
		00	01	11	10	
CD	00	1	0	0	1	D
	01	1	1	1	1	
	11	1	1	1	1	
	10	1	0	0	1	

4/18/2017

Sacramento State - Cook - CS&E 28 - Fall 2016

83

Tips

- There is no magic way to do Step 2. Look and play around until you find the answer
- You can overlap squares – just as long as you "cover" all the 1's




4/18/2017

Sacramento State - Cook - CS&E 28 - Fall 2016

84

Four-Variable K-Map

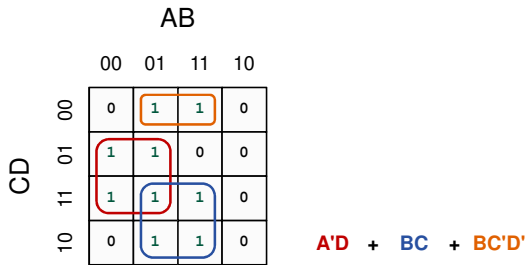

4/18/2017

Sacramento State - Cook - CSc 28 - Fall 2016

85

K-Maps Can Simplify Expressions

- The following is a complex expression that, on the surface, looks difficult to simplify
- K-Maps can help simplify expressions.

```
if (a && !b && c || a && b && !c ||
    a && !b && !c || a && b && c)
```

4/18/2017

Sacramento State - Cook - CSc 28 - Fall 2016

86

K-Maps Can Simplify Expressions

- The following is a complex expression that, on the surface, looks difficult to simplify
- K-Maps can help simplify expressions.


$ab'c' + abc' + ab'c + abc$

4/18/2017

Sacramento State - Cook - CSc 28 - Fall 2016

87

K-Maps Can Simplify Expressions

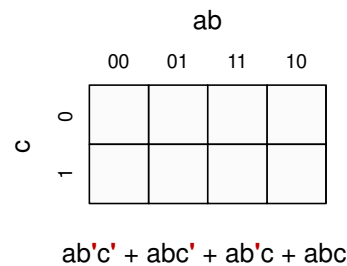


4/18/2017

Sacramento State - Cook - CSc 28 - Fall 2016

88

K-Maps Can Simplify Expressions

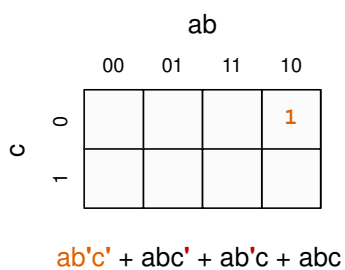


4/18/2017

Sacramento State - Cook - CSc 28 - Fall 2016

89

K-Maps Can Simplify Expressions

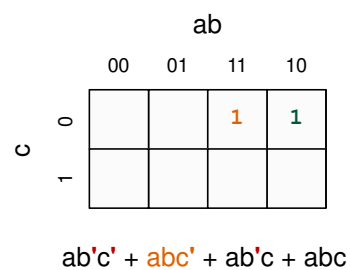

4/18/2017

Sacramento State - Cook - CSc 28 - Fall 2016

90

K-Maps Can Simplify Expressions

		ab			
		00	01	11	10
c	0			1	1
	1				1

$$ab'c' + abc' + ab'c + abc$$

4/18/2017

Sacramento State - Cook - CSc 28 - Fall 2016

91

K-Maps Can Simplify Expressions

		ab			
		00	01	11	10
c	0			1	1
	1			1	1

$$ab'c' + abc' + ab'c + abc$$

4/18/2017

Sacramento State - Cook - CSc 28 - Fall 2016

92

K-Maps Can Simplify Expressions

		ab			
		00	01	11	10
c	0			1	1
	1			1	1

$$ab'c' + abc' + ab'c + abc = a$$

4/18/2017

Sacramento State - Cook - CSc 28 - Fall 2016

93

Efficiency of K-Maps

- A K-Map does not necessarily make the *best* expression/circuit
- All expressions made this way are sums-of-products and some can be made simpler
- e.g. $a(b+c)$ is the same as $ab+ac$, but uses fewer gate inputs

4/18/2017

Sacramento State - Cook - CSc 28 - Fall 2016

94




Don't Care

When the Result is Meaningless

Don't Care

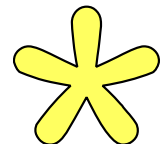- Sometimes *we don't really care* what output the circuit generates for some combinations of inputs
- So, for those inputs, the results are simply not significant




4/18/2017

Sacramento State - Cook - CSc 28 - Fall 2016

96

Don't Care

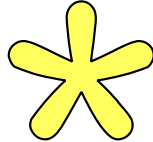- In truth tables, the value "Don't Care" is represented with an asterisk
- It can be considered True or False – whichever is more *convenient* for the circuit




4/18/2017

Sacramento State - Cook - CSc 28 - Fall 2016

97

Karnaugh Maps and Don't Care

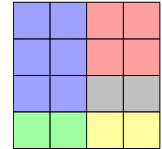- We can construct a Karnaugh Map like before
- Except the squares corresponding to don't care outputs are marked (with an asterisk)



4/18/2017

Sacramento State - Cook - CSc 28 - Fall 2016

98

Karnaugh Maps and Don't Care

- Then, when outlining blocks, we can (at our convenience) consider the "don't care" squares as either 0 or 1
- Since we want to make the largest outlines possible, we will sometimes consider a don't care to be true, and sometimes false

4/18/2017

Sacramento State - Cook - CSc 28 - Fall 2016

99

Example

- We want to guarantee that the output of a circuit is 1 if both inputs are 1
- And 0 when both inputs are 0
- But otherwise we do not care

4/18/2017

Sacramento State - Cook - CSc 28 - Fall 2016

100

Example


x	y	out
0	0	0
0	1	*
1	0	*
1	1	1

4/18/2017

Sacramento State - Cook - CSc 28 - Fall 2016

101

K-Map For The Example

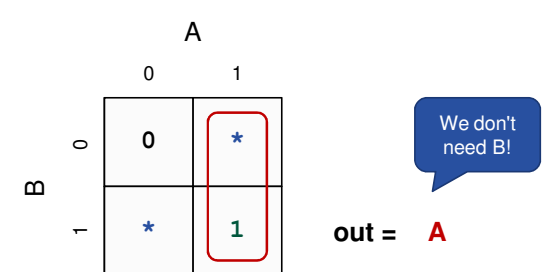

4/18/2017

Sacramento State - Cook - CSc 28 - Fall 2016

102

... or we can do this

	A	
	0	1
B	0	*
1	*	1

out = **B**

Just B!

4/18/2017

Sacramento State - Cook - CS&E 28 - Fall 2016

103

Four-Variable (with Don't Care)

		AB			
		00	01	11	10
CD	0	0	1	1	*
	01	1	1	*	0
	11	1	1	1	0
	10	*	1	1	0

out = **B + A'D**

4/18/2017

Sacramento State - Cook - CS&E 28 - Fall 2016

104



Functional Completeness

Just How Much Do We Need?

Functional Completeness

- We can construct a circuit for any Boolean expression using **and** / **or** / **not**
- This means the set of gates {and, or, not} is *functionally complete*



4/18/2017

Sacramento State - Cook - CS&E 28 - Fall 2016

106

Function Completeness

- However, we don't need all three gates
- DeMorgan's laws shows us that we can construct:
 - an OR using an AND
 - and AND using an OR



4/18/2017

Sacramento State - Cook - CS&E 28 - Fall 2016

107

We Don't Need Or!

- So {and, not} are also complete because by DeMorgan's Law:

$$x + y = (x'y')'$$
- So, any expression that can be written using {**and**, **or**, **not**} can be written using just {**and**, **not**}



4/18/2017

Sacramento State - Cook - CS&E 28 - Fall 2016

108

or... We Don't Need And!

- Also {or, not} is functionally complete since $xy = (x' + y)'$
- So, any expression that can be written using {and, or, not} can be written using just {or, not}



4/18/2017

Sacramento State - Cook - CSc 28 - Fall 2016

109

Functional Completeness

- So, are any of the singular sets {and}, {or}, {not} functionally complete?
- In other words, can and/or/not all be converted into a single type of gate?
- No.** Neither {and} or {or} can be converted to a {not}

4/18/2017

Sacramento State - Cook - CSc 28 - Fall 2016

110

NAND

- So, is there a gate that can, alone, be functional complete?
- What about NAND (negated And)?
 - $x \text{ nand } y = (xy)'$
 - Note: the NAND gate is not implemented with an AND gate and a NOT gate. It just has the same truth table as $(xy)'$

4/18/2017

Sacramento State - Cook - CSc 28 - Fall 2016

111

NAND

- To show that {nand} is functionally complete, we need to show that we can implement {and, or, not} using it
- The result would be greatly beneficial!
 - we would have to just construct 1 gate to create any circuit
 - this would greatly aid construction

4/18/2017

Sacramento State - Cook - CSc 28 - Fall 2016

112

Not → Nand

Converting not to nand:

$$\begin{aligned}
 x' &= x' \\
 &= (xx)' && \text{Idempotent} \\
 &= x \text{ nand } x && \text{nand format}
 \end{aligned}$$

We can implement NOT by using a NAND.
Both input will be x

4/18/2017

Sacramento State - Cook - CSc 28 - Fall 2016

113

Or → Nand

Note: $x' = x \text{ nand } x$

$$\begin{aligned}
 x + y &= x + y \\
 &= (x'y')' && \text{DeMorgan} \\
 &= x' \text{ nand } y' && \text{nand format} \\
 &= (x \text{ nand } x) \text{ nand } (y \text{ nand } y)
 \end{aligned}$$

Last proof let us convert
NOT into NAND

4/18/2017

Sacramento State - Cook - CSc 28 - Fall 2016

114

And \rightarrow Nand

Note: $x' = x \text{ nand } x$

$$\begin{aligned} xy &= xy \\ &= (x \text{ nand } y)' && \text{Negate nand} \\ &= (x \text{ nand } y) \text{ nand } (x \text{ nand } y) \end{aligned}$$

Last proof let us convert
NOT into NAND

4/18/2017

Sacramento State - Cook - CSc 28 - Fall 2016

115

Summary

- The expressions below show that nand can be used to implement NOT, OR, AND
- So, we can just use NAND since it is *functionally complete*

$$\begin{aligned} x' &= x \text{ nand } x \\ xy &= (x \text{ nand } y) \text{ nand } (x \text{ nand } y) \\ x + y &= (x \text{ nand } x) \text{ nand } (y \text{ nand } y) \end{aligned}$$


4/18/2017

Sacramento State - Cook - CSc 28 - Fall 2016

116

How Hardware Works

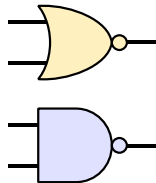- Also NOR is functionally complete
- $P \text{ NOR } Q = (P + Q)'$
- Hardware can alternatively use this gate rather than NAND




4/18/2017

Sacramento State - Cook - CSc 28 - Fall 2016

117

How Hardware Works

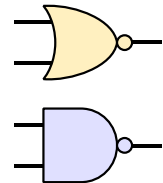- If our hardware can just implement NAND or NOR, then we can create a circuit with just one gate
- In fact, many fabrication processes use only NAND or NOR gates



4/18/2017

Sacramento State - Cook - CSc 28 - Fall 2016

118