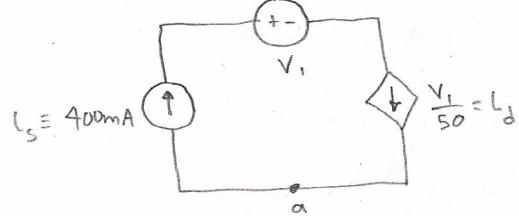


HOMEWORK #2

Problems 1-9

Problem 2.6 in text

1:) Given the following circuit



$$a) \text{ Define } I_s = 400\text{mA}, \quad l_d = \frac{V_1}{50}$$

Using KCL at node a, labeled above:

$$\begin{array}{c} \text{a} \\ \text{---} \\ \text{---} \\ \text{I}_s \quad \text{l}_d \end{array} \quad \sum I_{\text{in}} = \sum I_{\text{out}}$$

(i) $l_d = I_s$

$$\frac{V_1}{50} = 400\text{mA} \quad V_1 = 50(400 \times 10^{-3})$$

$$V_1 = 20000 \times 10^{-3} \text{V}$$

$$V_1 = 20\text{V}$$

$$b) \quad I_1 = 400\text{mA}$$


$$V_1$$

$$P_1 = +V_1 I_1 = + (400\text{mA})(20\text{V}) = 8000\text{mW}$$

$$P_1 = 8.0\text{W} \quad \text{absorbed/dissipated}$$

Problem 2.12 in text


2:) Given the following circuit

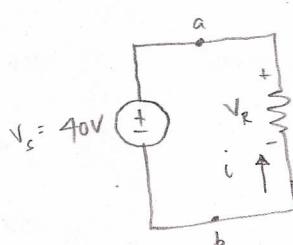

a) Label the voltage across the resistor as V_R with the polarity shown. With this $V_R = +40\text{V}$. Also by the passive sign convention, $V_R = -iR$. $i = -\frac{V_R}{R}$

$$i = -\frac{40\text{V}}{2.5 \times 10^3 \Omega} = -16 \times 10^{-4} \text{A} = -0.016\text{A} = l$$

b) For the power supplied by the source:

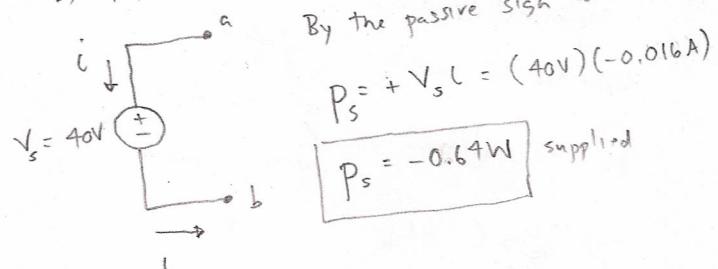


By the passive sign convention

$$P_s = +V_s l = (40\text{V})(-0.016\text{A})$$

$$P_s = -0.64\text{W} \quad \text{supplied}$$

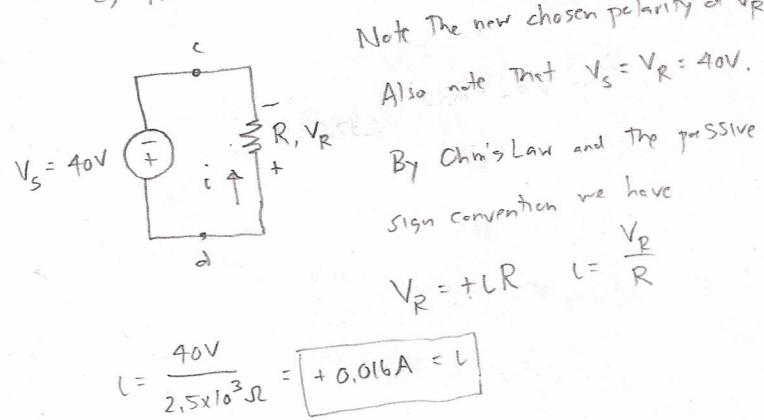c) Reverse the polarity of the voltage source



Note the new chosen polarity of V_R . Also note that $V_s = V_R = 40\text{V}$.


By Ohm's Law and the passive sign convention we have

$$V_R = +iR \quad i = \frac{V_R}{R}$$

$$i = \frac{40\text{V}}{2.5 \times 10^3 \Omega} = +0.016\text{A} = l$$

For the power supplied by the source:

By the passive sign convention

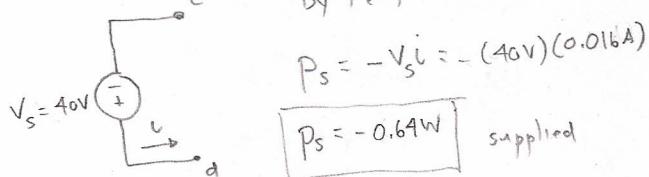


$$P_s = -V_s l = - (40\text{V})(0.016\text{A})$$


$$P_s = -0.64\text{W} \quad \text{supplied}$$

Problem 2.18 in text

3) Given the following circuit

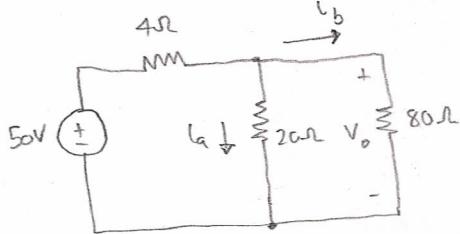

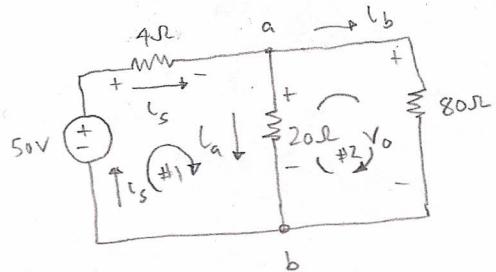Define a current i_s as follows and add the following voltage polarities across the resistors as follows.



Note that i_s passes through the voltage source AND the 4Ω resistor.

$$\text{Using KCL at node } a: \sum_{\text{node } a} i_{in} = \sum_{\text{node } a} i_{out}$$

$$(1) i_s = i_a + i_b$$

By Ohms Law applied to each resistor we have

$$V_{4\Omega} = +i_s(4\Omega) = 4i_s$$

$$V_{20\Omega} = +i_a(20\Omega) = 20i_a$$

$$V_{80\Omega} = +i_b(80\Omega) = 80i_b$$

Using KVL around loop #1 labeled above

$$(2) -50V + 4i_s + 20i_a = 0$$

$$4i_s + 20i_a = 50$$

Using KVL around loop #2 labeled above

$$(3) -20i_a + 80i_b = 0$$

solving for i_a

$$20i_a = 80i_b$$

$$i_a = 4i_b$$

The system of equations we have to solve is

$$(1) i_s = i_a + i_b$$

$$(2) 4i_s + 20i_a = 50$$

$$(3) i_a = 4i_b$$

This is a system of 3 equations and three unknowns.

Use (1) to eliminate i_a from (2)

$$4(i_a + i_b) + 20i_a = 50$$

$$(4) 24i_a + 4i_b = 50$$

Use (3) to eliminate i_a from (4)

$$24(4i_b) + 4i_b = 50$$

$$96i_b + 4i_b = 50$$

$$b) 100i_b = 50$$

$$i_b = 0.5A$$

Also $i_a = 4i_b$ from (3). But $i_b = 0.5A$ so

$$a) i_a = 4(0.5A) = 2.0A = i_a$$

c) Using Ohm's Law by looking at the 80Ω resistor

$$\begin{array}{c} \xrightarrow{i_b = 0.5A} \\ a \xrightarrow{+} \\ \left. \begin{array}{c} \\ 80\Omega \\ \hline V_o \end{array} \right. \\ b \xrightarrow{-} \end{array} \quad V_o = i_b R_{80\Omega}$$

$$V_o = (0.5A)(80\Omega) = 40V$$

$$V_o = +40V$$

d) For each resistor use the passive sign convention

$$\text{and } P = IV, P = I^2 R, P = \frac{V^2}{R}$$

$$P_{4\Omega} = +i_s^2 R_{4\Omega} \text{ but by (1) } i_s = i_a + i_b = 2.5A$$

$$P_{4\Omega} = + (2.5A)^2 (4\Omega) = +25W = P_{4\Omega}$$

$$P_{20\Omega} = i_a^2 R_{20\Omega} = (2.0A)^2 (20\Omega) = +80W = P_{20\Omega}$$

$$P_{80\Omega} = i_b^2 R_{80\Omega} = (0.5A)^2 (80\Omega) = +20W = P_{80\Omega}$$


$$e) P_{50V} = -i_s V_{50V} = -(2.5A)(50V) = -125W = P_{50V}$$

HOMEWORK #2


Problems 1-9

Problem 2.23 in text

4:) Given the following circuit along with

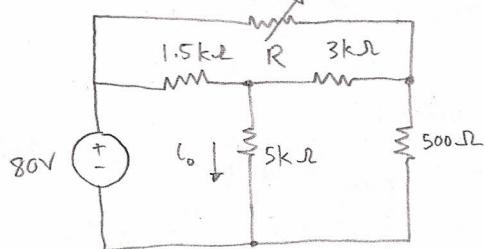 $I_o = 10\text{mA}$. Determine the value of R .

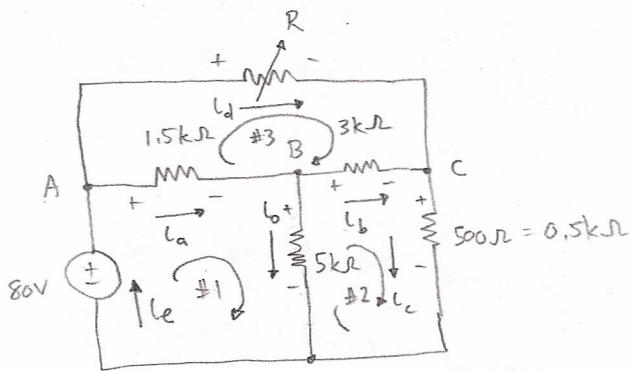Define the following currents, loops and nodes



With these definitions we can apply Ohm's Law.

to each resistor noting the passive sign convention

$$\text{as } V_a = 1.5I_a, V_b = +3I_b, V_c = +0.5I_c$$

 $V_d = I_d R, \quad V_o = 5I_o$ where all resistances are

in kΩ.

- Using KVL around loop #1:

$$(1) -80V + 1.5I_a + 5I_o = 0$$

$$1.5I_a = 80 - 5I_o$$

$$I_a = \frac{80 - 5I_o}{1.5} \quad \text{but } I_o = 10\text{mA}$$

$$I_a = \frac{80V - (5\text{k}\Omega)(10\text{mA})}{1.5\text{k}\Omega} = \frac{80 - 50}{1.5} = 20\text{mA}$$

- Using KCL at node B:

$$I_a = I_o + I_b \quad \text{but } I_o = 10\text{mA}, I_a = 20\text{mA}$$

$$\text{so } I_b = I_a - I_o = 20\text{mA} - 10\text{mA} = 10\text{mA} = I_o$$

- Using KVL around loop #3:

$$I_d R - 3I_b - 1.5I_a = 0$$

$$\text{But } I_a = 20\text{mA}, I_b = 10\text{mA}$$

$$I_d R - (3\text{k}\Omega)(10\text{mA}) - (1.5\text{k}\Omega)(20\text{mA}) = 0$$

$$(3) I_d R = 30V + 30V = 60V \quad R = \frac{60V}{I_d}$$

Using KCL at node C:

$$(4) I_b + I_d = I_c \quad \text{but } I_b = 10\text{mA}$$

$$10\text{mA} + I_d = I_c, \quad \text{or } 10 + I_d = I_c$$

Using KVL around loop #2:

$$-5I_o + 3I_b + 0.5I_c = 0$$

$$\text{But } I_o = 10\text{mA}, I_b = 10\text{mA}$$

$$-(5\text{k}\Omega)(10\text{mA}) + (3\text{k}\Omega)(10\text{mA}) + \frac{1}{2}I_c = 0$$

$$-50V + 30V = -\frac{1}{2}I_c \quad I_c = +40\text{mA}$$

Calculations: Use $I_c = 40\text{mA}$ in (4) above

$$10\text{mA} + I_d = I_c \quad 10\text{mA} + I_d = 40\text{mA}$$


$$I_d = 30\text{mA}$$

Use this value in (3) above $R = \frac{60V}{I_d}$


$$R = \frac{60V}{30\text{mA}} = 2\text{k}\Omega \quad \text{so } \boxed{R = 2\text{k}\Omega}$$

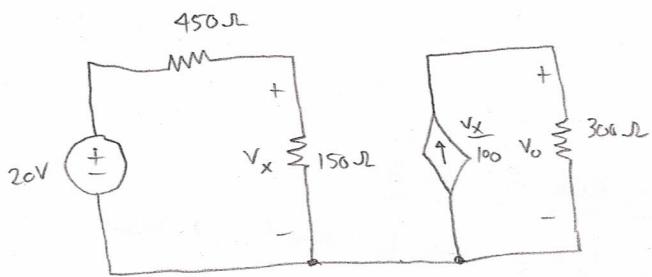Problem 2.33 in text

5c) For the given circuit, find V_o and P_{absorbed}



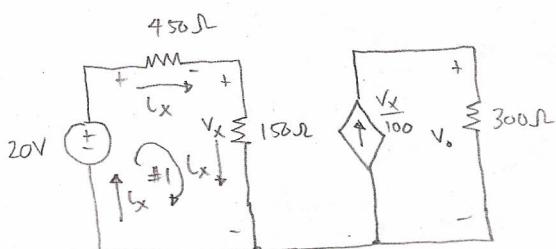Define a current I_x in the diagram below



Note I_x passes through the 20V source, the 450Ω resistor and the 150Ω resistor.

Using KVL around loop #1:

$$-20 + 450I_x + 150I_x = 0$$

$$600I_x = 20 \quad I_x = \frac{1}{30} \text{ A}$$

Ohm's Law on the 150Ω resistor:

$$V_x = +I_x R_{150\Omega} = \left(\frac{1}{30}\text{A}\right)(150\Omega) = 5\text{V}$$


Dependent source current: Since $V_x = 5\text{V}$, the

current provided by the dependent source

$$I_{\text{source}} = \frac{V_x}{100} = \frac{5\text{V}}{100} = \frac{1}{20} \text{ A}$$

Looking at the 300Ω resistor:
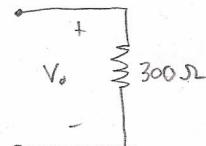
$$\rightarrow I_{\text{source}} = \frac{1}{20} \text{ A} \quad V_o = +I_{\text{source}} R_{300\Omega}$$



$$V_o = \left(\frac{1}{20}\text{A}\right)(300\Omega)$$

$$V_o = +\frac{30}{2}\text{V} = 15\text{V}$$

$$\boxed{V_o = 15\text{V}}$$

b) Note that the resistors will absorb power

$$P_{450\Omega} = I_x^2 R_{450\Omega} = \left(\frac{1}{30}\text{A}\right)^2 (450\Omega) = +0.5\text{W}$$

$$P_{150\Omega} = I_x^2 R_{150\Omega} = \left(\frac{1}{30}\text{A}\right)^2 (150\Omega) = \frac{1}{6}\text{W}$$

$$P_{150\Omega} = 0.1667\text{W}$$

$$P_{300\Omega} = \frac{V_o^2}{R_{300\Omega}} = \frac{(15\text{V})^2}{300\Omega} = 0.75\text{W}$$

For the sources:

$$P_{20V} = -I_x V_{20V} = -\left(\frac{1}{30}\text{A}\right)(20\text{V})$$

$$P_{20V} = -\frac{2}{3}\text{W} = -0.6667\text{W}$$

$$P_{\text{dep}} = -I_d V_o = -\frac{V_x}{100} V_o$$

$$\text{but } V_x = 5\text{V}, V_o = 15\text{V}$$

$$P_{\text{dep}} = -\left(\frac{5}{100}\right)(15) = -0.75\text{W}$$

$$P_{\text{absorbed}} = P_{450\Omega} + P_{150\Omega} + P_{300\Omega}$$

$$P_{\text{absorbed}} = 0.5\text{W} + 0.1667\text{W} + 0.75\text{W}$$

$$P_{\text{absorbed}} = 1.4167\text{W}$$

$$P_{\text{generated}} = P_{20V} + P_{\text{dep}} = -0.6667\text{W} - 0.75\text{W}$$

$$P_{\text{generated}} = -1.4167\text{W}$$

P 2.12 [a] Using the passive sign convention and Ohm's law,

$$i = -\frac{v}{R} = -\frac{40}{2500} = -0.016 = -16 \text{ mA}$$


[b] $P_R = Ri^2 = (2500)(-0.016)^2 = 0.64 = 640 \text{ mW}$

[c] Using the passive sign convention with the voltage polarity reversed,

$$i = \frac{v}{R} = \frac{40}{2500} = 0.016 = 16 \text{ mA}$$

$$P_R = Ri^2 = (2500)(0.016)^2 = 0.64 = 640 \text{ mW}$$

P 2.18 [a]

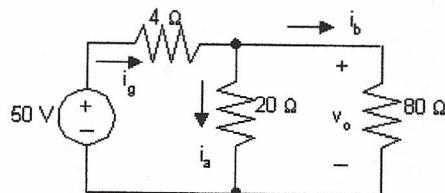

$$20i_a = 80i_b \quad i_g = i_a + i_b = 5i_b$$

$$i_a = 4i_b$$

$$50 = 4i_g + 80i_b = 20i_b + 80i_b = 100i_b$$

$$i_b = 0.5 \text{ A}, \text{ therefore, } i_a = 2 \text{ A} \quad \text{and} \quad i_g = 2.5 \text{ A}$$

[b] $i_b = 0.5 \text{ A}$

[c] $v_o = 80i_b = 40 \text{ V}$

2-18 CHAPTER 2. Circuit Elements

[d] $p_{4\Omega} = i_g^2(4) = 6.25(4) = 25 \text{ W}$

$$p_{20\Omega} = i_a^2(20) = (4)(20) = 80 \text{ W}$$

$$p_{80\Omega} = i_b^2(80) = 0.25(80) = 20 \text{ W}$$


[e] $p_{50V} \text{ (delivered)} = 50i_g = 125 \text{ W}$

Check:

$$\sum P_{\text{dis}} = 25 + 80 + 20 = 125 \text{ W}$$

$$\sum P_{\text{del}} = 125 \text{ W}$$

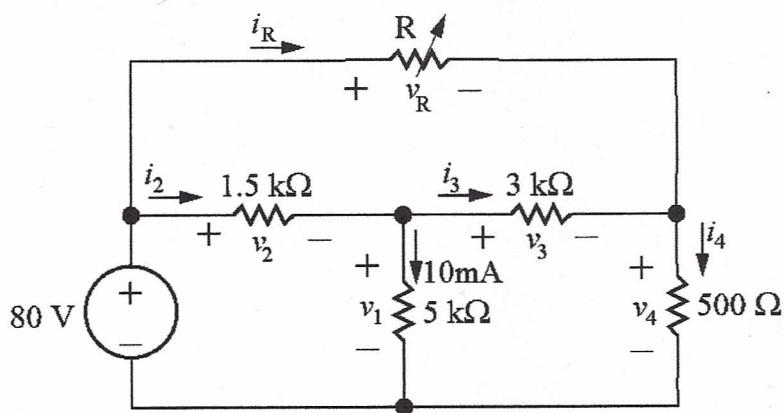P 2.23 Label all unknown resistor voltages and currents:



$$\text{Ohms' law for } 5 \text{ k}\Omega \text{ resistor: } v_1 = (0.01)(5000) = 50 \text{ V}$$

$$\text{KVL for lower left loop: } -80 + v_2 + 50 = 0 \rightarrow v_2 = 80 - 50 = 30 \text{ V}$$

$$\text{Ohm's law for } 1.5 \text{ k}\Omega \text{ resistor: } i_2 = v_2/1500 = 30/1500 = 20 \text{ mA}$$

KCL at center node:

$$i_2 = i_3 + 0.01 \rightarrow i_3 = i_2 - 0.01 = 0.02 - 0.01 = 0.01 = 10 \text{ mA}$$

$$\text{Ohm's law for } 3 \text{ k}\Omega \text{ resistor } v_3 = 3000i_3 = 3000(0.01) = 30 \text{ V}$$

KVL for lower right loop:

$$-v_1 + v_3 + v_4 = 0 \rightarrow v_4 = v_1 - v_3 = 50 - 30 = 20 \text{ V}$$

Problems 2-21

$$\text{Ohm's law for } 500 \Omega \text{ resistor: } i_4 = v_4/500 = 20/500 = 0.04 = 40 \text{ mA}$$

KCL for right node:

$$i_3 + i_R = i_4 \rightarrow i_R = i_4 - i_3 = 0.04 - 0.01 = 0.03 = 30 \text{ mA}$$


KVL for outer loop:

$$-80 + v_R + v_4 = 0 \rightarrow v_R = 80 - v_4 = 80 - 20 = 60 \text{ V}$$

Therefore,

$$R = \frac{v_R}{i_R} = \frac{60}{0.03} = 2000 = 2 \text{ k}\Omega$$

P 2.33 Label unknown current:

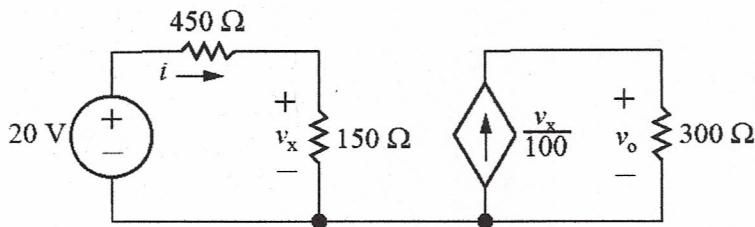

$$-20 + 450i + 150i = 0 \quad (\text{KVL and Ohm's law})$$

$$\text{so } 600i = 20 \rightarrow i = 33.33 \text{ mA}$$

$$v_x = 150i = 150(0.0333) = 5 \text{ V} \quad (\text{Ohm's law})$$

$$v_o = 300 \left(\frac{v_x}{100} \right) = 300(5/100) = 15 \text{ V} \quad (\text{Ohm's law})$$

Calculate the power for all components:

$$p_{20V} = -20i = -20(0.0333) = -0.667 \text{ W}$$

$$p_{d.s.} = -v_o \left(\frac{v_x}{100} \right) = -(15)(5/100) = -0.75 \text{ W}$$

$$p_{450} = 450i^2 = 450(0.033)^2 = 0.5 \text{ W}$$

$$p_{150} = 150i^2 = 150(0.033)^2 = 0.1667 \text{ W}$$

$$p_{300} = \frac{v_o^2}{300} = \frac{15^2}{300} = 0.75 \text{ W}$$

Thus the total power absorbed is

$$p_{\text{abs}} = 0.5 + 0.1667 + 0.75 = 1.4167 \text{ W}$$

P 2.36 [a] $-50 - 20i_\sigma + 18i_\Delta = 0$

$$-18i_\Delta + 5i_\sigma + 40i_\sigma = 0 \quad \text{so} \quad 18i_\Delta = 45i_\sigma$$

$$\text{Therefore, } -50 - 20i_\sigma + 45i_\sigma = 0, \quad \text{so} \quad i_\sigma = 2 \text{ A}$$

$$18i_\Delta = 45i_\sigma = 90; \quad \text{so} \quad i_\Delta = 5 \text{ A}$$

$$v_o = 40i_\sigma = 80 \text{ V}$$

- [b] i_g = current out of the positive terminal of the 50 V source
 v_d = voltage drop across the $8i_\Delta$ source

$$i_g = i_\Delta + i_\sigma + 8i_\Delta = 9i_\Delta + i_\sigma = 47 \text{ A}$$

$$v_d = 80 - 20 = 60 \text{ V}$$

$$\sum P_{\text{gen}} = 50i_g + 20i_\sigma i_g = 50(47) + 20(2)(47) = 4230 \text{ W}$$

$$\begin{aligned} \sum P_{\text{diss}} &= 18i_\Delta^2 + 5i_\sigma(i_g - i_\Delta) + 40i_\sigma^2 + 8i_\Delta v_d + 8i_\Delta(20) \\ &= (18)(25) + 10(47 - 5) + 4(40) + 40(60) + 40(20) \\ &= 4230 \text{ W}; \quad \text{Therefore,} \end{aligned}$$

$$\sum P_{\text{gen}} = \sum P_{\text{diss}} = 4230 \text{ W}$$

- P 3.5 Always work from the side of the circuit furthest from the source. Remember that the current in all series-connected circuits is the same, and that the voltage drop across all parallel-connected resistors is the same.

[a] Circuit in Fig. P3.3(a):

$$\begin{aligned} R_{\text{eq}} &= [(7000 + 5000)\parallel 6000] + 8000 = 12,000\parallel 6000 + 8000 \\ &= 4000 + 8000 = 12 \text{ k}\Omega \end{aligned}$$

Circuit in Fig. P3.3(b):

$$\begin{aligned} R_{\text{eq}} &= [500\parallel(800 + 1200)] + 300 + 200 = (500\parallel 2000) + 300 + 200 \\ &= 400 + 300 + 200 = 900 \Omega \end{aligned}$$

Circuit in Fig. P3.3(c):

$$R_{\text{eq}} = (35 + 15 + 25)\parallel(10 + 40) = 75\parallel 50 = 30 \Omega$$

Circuit in Fig. P3.3(d):

$$\begin{aligned} R_{\text{eq}} &=([(70 + 80)\parallel 100] + 50 + 90)\parallel 300 = [(150\parallel 100) + 50 + 90]\parallel 300 \\ &= (60 + 50 + 90)\parallel 300 = 200\parallel 300 = 120 \Omega \end{aligned}$$

- [b] Note that in every case, the power delivered by the source must equal the power absorbed by the equivalent resistance in the circuit. For the circuit in Fig. P3.3(a):

$$P = \frac{V_s^2}{R_{\text{eq}}} = \frac{18^2}{12,000} = 0.027 = 27 \text{ mW}$$

For the circuit in Fig. P3.3(b):

$$P = \frac{V_s^2}{R_{\text{eq}}} = \frac{27^2}{900} = 0.81 = 810 \text{ mW}$$

For the circuit in Fig. P3.3(c):

$$P = \frac{V_s^2}{R_{\text{eq}}} = \frac{90^2}{30} = 270 \text{ W}$$

For the circuit in Fig. P3.3(d):

$$P = I_s^2(R_{\text{eq}}) = (0.03)^2(120) = 0.108 = 108 \text{ mW}$$

- P 3.9 Write an expression for the resistors in series and parallel from the right side of the circuit to the left. Then simplify the resulting expression from left to right to find the equivalent resistance.

[a] $R_{ab} = [(26 + 10)\parallel 18 + 6]\parallel 36 = (36\parallel 18 + 6)\parallel 36 = (12 + 6)\parallel 36 = 18\parallel 36 = 12 \Omega$

[b] $R_{ab} = [(12 + 18)\parallel 10\parallel 15\parallel 20 + 16]\parallel 30 + 4 + 14 = (30\parallel 10\parallel 15\parallel 20 + 16)\parallel 30 + 4 + 14 = (4 + 16)\parallel 30 + 4 + 14 = 20\parallel 30 + 4 + 14 = 12 + 4 + 14 = 30 \Omega$

[c] $R_{ab} = (500\parallel 1500\parallel 750 + 250)\parallel 2000 + 1000 = (250 + 250)\parallel 2000 + 1000 = 500\parallel 2000 + 1000 = 400 + 1000 = 1400 \Omega$

- [d] Note that the wire on the far right of the circuit effectively removes the 60Ω resistor!

$$\begin{aligned} R_{ab} &= [([(30 + 18)\parallel 16 + 28]\parallel 40 + 20)\parallel 24 + 25 + 10]\parallel 50 \\ &=([(48\parallel 16 + 28)\parallel 40 + 20]\parallel 24 + 25 + 10)\parallel 50 \\ &=([(12 + 28)\parallel 40 + 20]\parallel 24 + 25 + 10)\parallel 50 = [(40\parallel 40 + 20)\parallel 24 + 25 + 10]\parallel 50 \\ &= [(20 + 20)\parallel 24 + 25 + 10]\parallel 50 = (40\parallel 24 + 25 + 10)\parallel 50 = (15 + 25 + 10)\parallel 50 \\ &= 50\parallel 50 = 25 \Omega \end{aligned}$$

P 3.12 [a] $v_o = \frac{160(3300)}{(4700 + 3300)} = 66 \text{ V}$

[b] $i = 160/8000 = 20 \text{ mA}$

$$P_{R_1} = (400 \times 10^{-6})(4.7 \times 10^3) = 1.88 \text{ W}$$

$$P_{R_2} = (400 \times 10^{-6})(3.3 \times 10^3) = 1.32 \text{ W}$$

- [c] Since R_1 and R_2 carry the same current and $R_1 > R_2$ to satisfy the voltage requirement, first pick R_1 to meet the 0.5 W specification

$$i_{R_1} = \frac{160 - 66}{R_1}, \quad \text{Therefore, } \left(\frac{94}{R_1}\right)^2 R_1 \leq 0.5$$

$$\text{Thus, } R_1 \geq \frac{94^2}{0.5} \quad \text{or} \quad R_1 \geq 17,672 \Omega$$

Now use the voltage specification:

$$\frac{R_2}{R_2 + 17,672}(160) = 66$$

$$\text{Thus, } R_2 = 12,408 \Omega$$